

Lecture 01B


Timing Analysis of Sequential Circuit



What is a sequential circuit

- Sequential Circuit:


 
- a digital circuit with **storage element** to **memorize** current **state**
- Figure 5-1:



- the counter part -- **Combinational Circuit**
 - a digital circuit without storage element

The key to design hardware



- imagine how a circuit works

 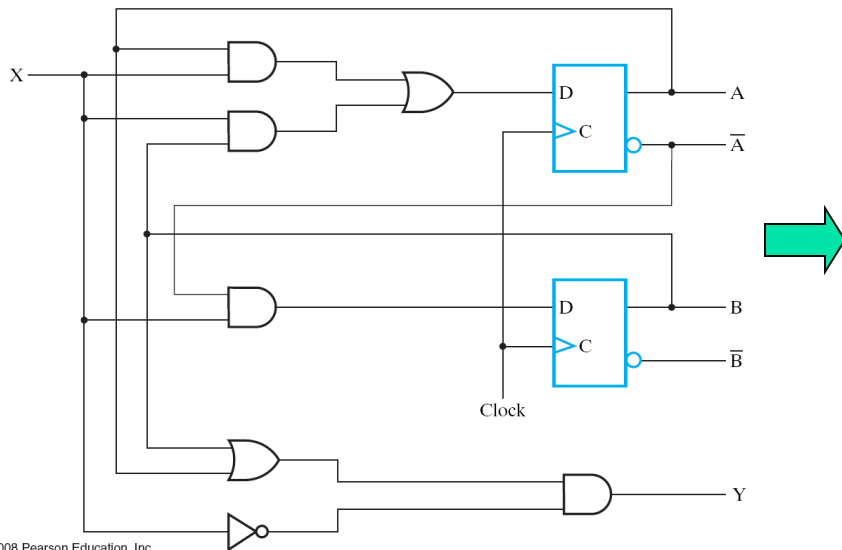



Note: we are talking about

Synchronous Clocked Circuit

  
- All flip flops receive the same clock signal



Cycle-based vs. Actual Timing

  

Actual Timing

 

Cycle-based reasoning





Analysis for actual timing

minimum clock period time



Core Question

 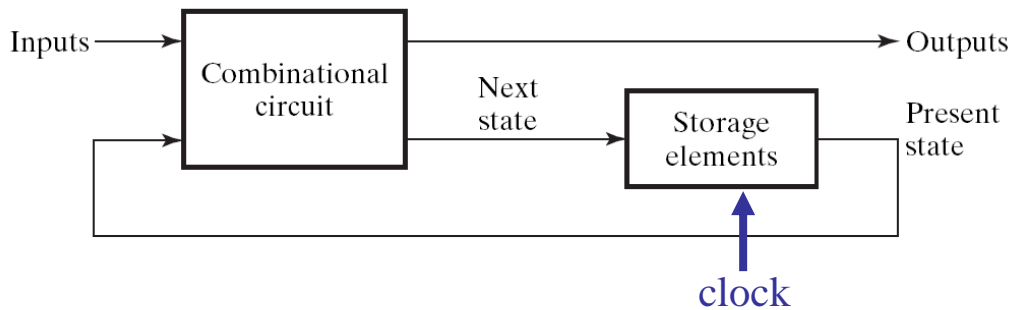- What's the minimum **clock period time** to make the circuit works correctly?




What's the clock for?

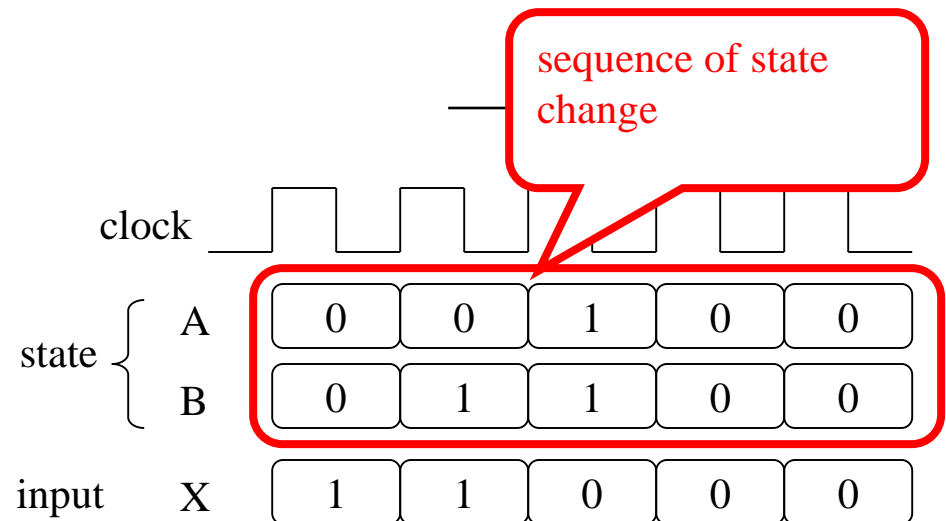 - Answer: to make the circuit doing **step-by-step** computation
 - clock signal is fed to all flip flops of the circuit
 - to let a sequential circuit performs its task in step-by-step manner
 - forms a **sequence of state change** on flip flops
 - imagine the flip flops as **variables** for programming



Core Question

 - What's the maximum **one-step** computation time?




$$\textit{delay}(A, B) \leq ?$$

the combinational circuit is to
perform one-step computation

Core Question

 
- What's the maximum **one-step** computation time?



the one-step computation time


$$\text{delay}(A, B) \leq ?$$

Recall: property of D flip-flop

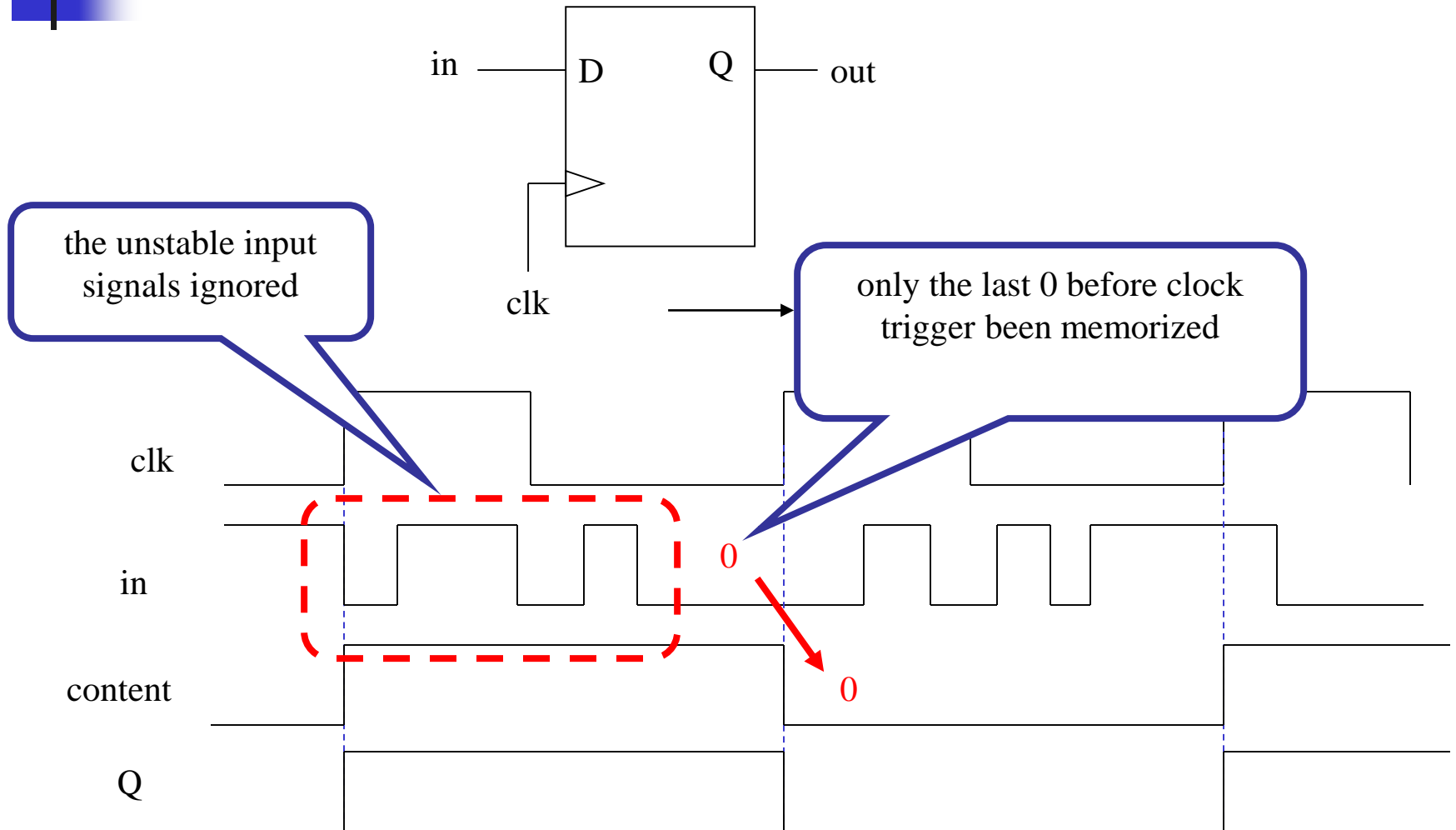

Core Question

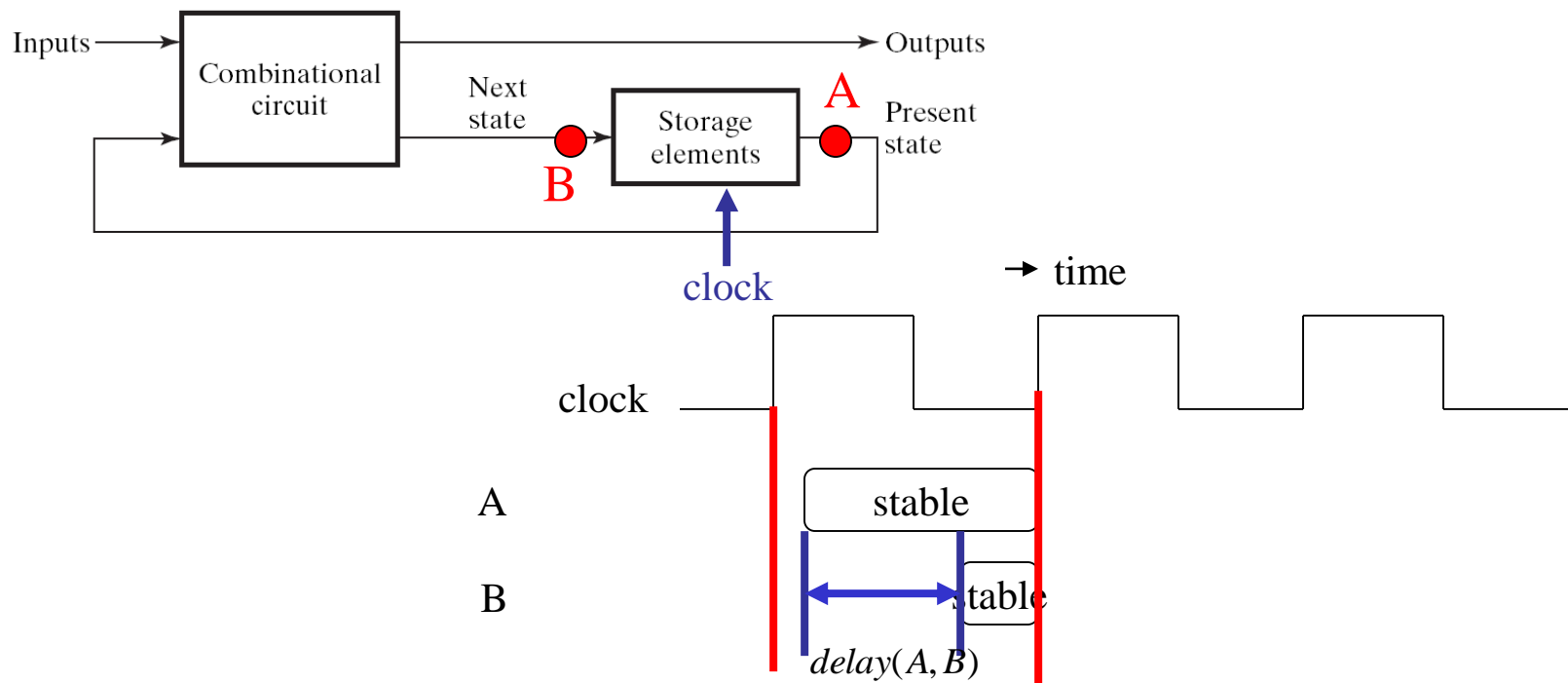- What's the maximum **one-step** computation time?
 $delay(A, B) \leq (\text{clock period time})$






Analysis Example

 
Problem Description

- find the maximum clock frequency (minimum clock period time) of the circuit


- delay of AND-gate: 3 ns
- delay of OR-gate: 4 ns
- setup time of D-FF: 2 ns
- clock-to-output time of D-FF: 1 ns



Delay of a gate

 


Delay for a flip-flop

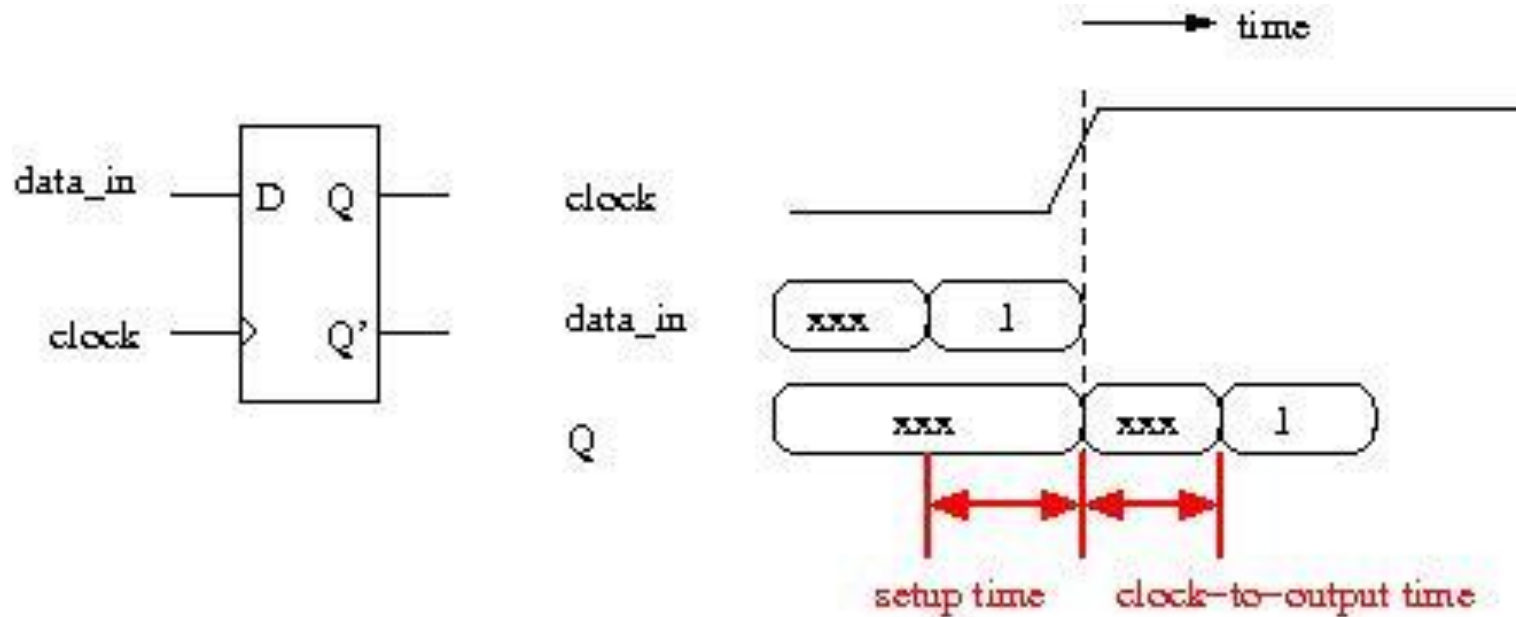

 Problem Description


- find the maximum clock frequency (minimum clock period time) of the circuit

- delay of AND-gate: 3 ns
- delay of OR-gate: 4 ns
- setup time of D-FF: 2 ns
- clock-to-output time of D-FF: 1 ns




Analysis method

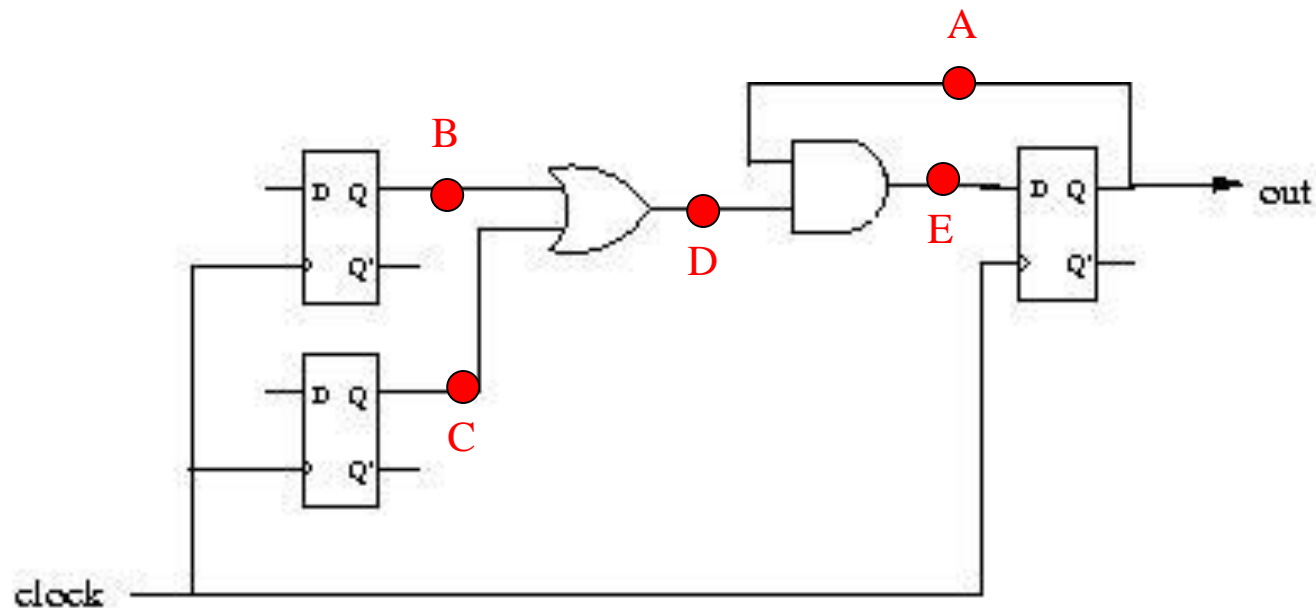- start from the outputs of D-FFs
- mark critical points in the circuit
- find-out signal stable time for each point




Timing analysis

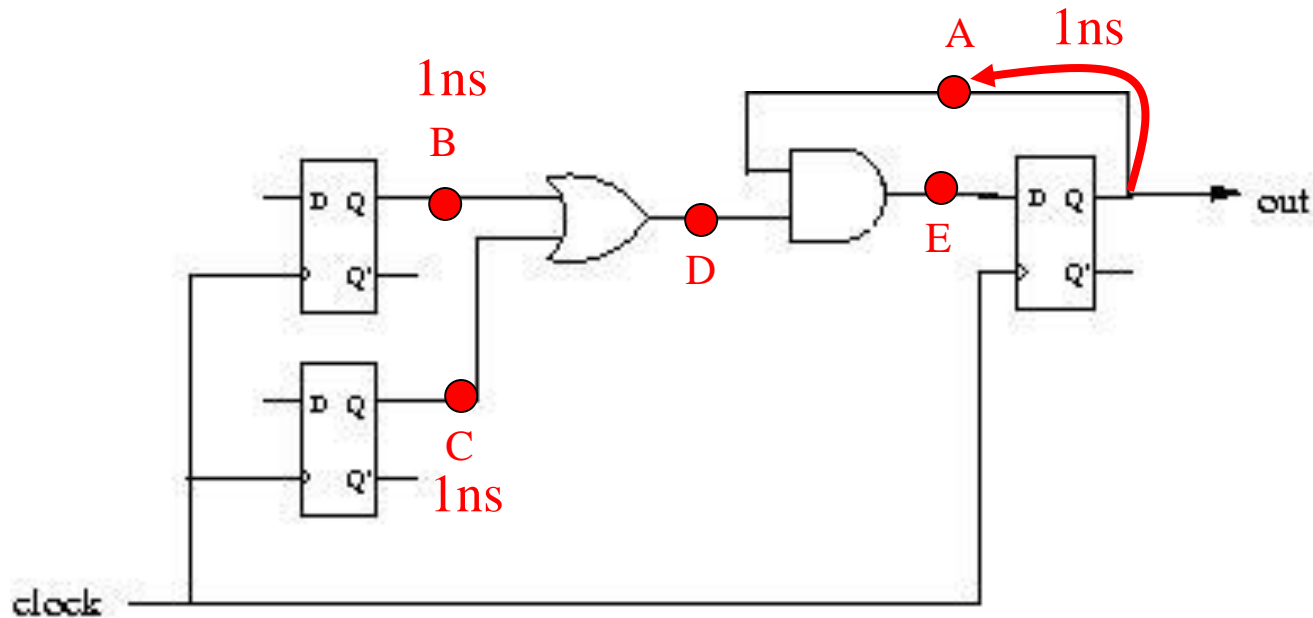- delay of AND-gate: 3 ns
- delay of OR-gate: 4 ns
- setup time of D-FF: 2 ns
- clock-to-output time of D-FF: 1 ns




Timing analysis

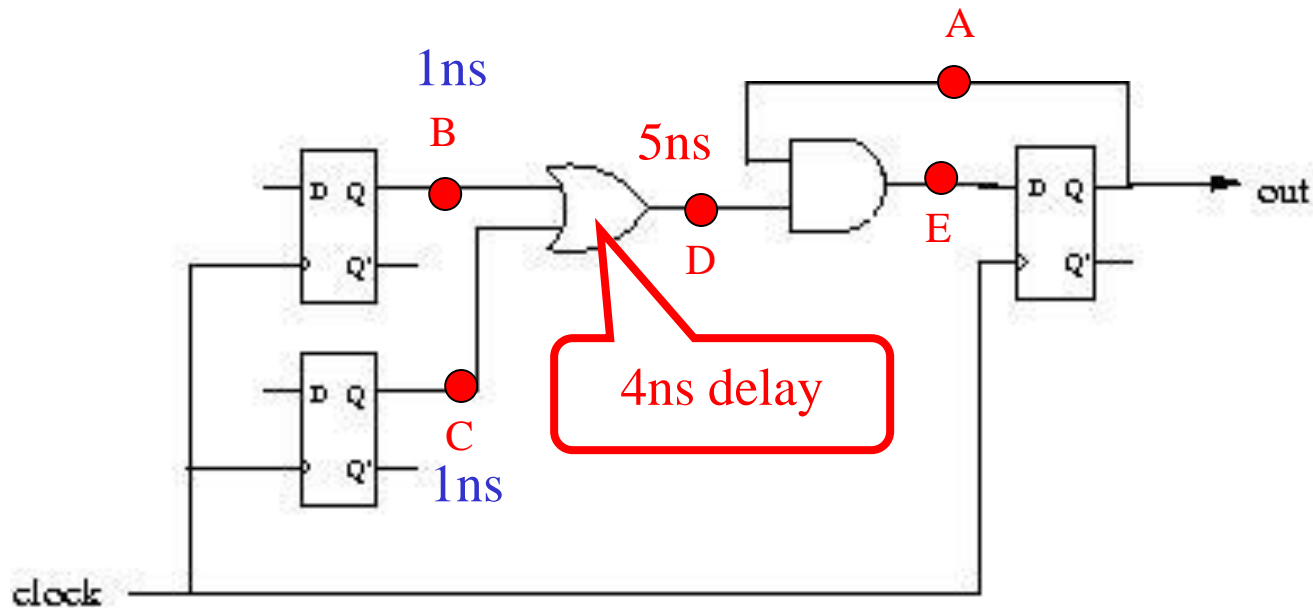- delay of AND-gate: 3 ns
- delay of OR-gate: 4 ns
- setup time of D-FF: 2 ns
- clock-to-output time of D-FF: 1 ns




Timing analysis

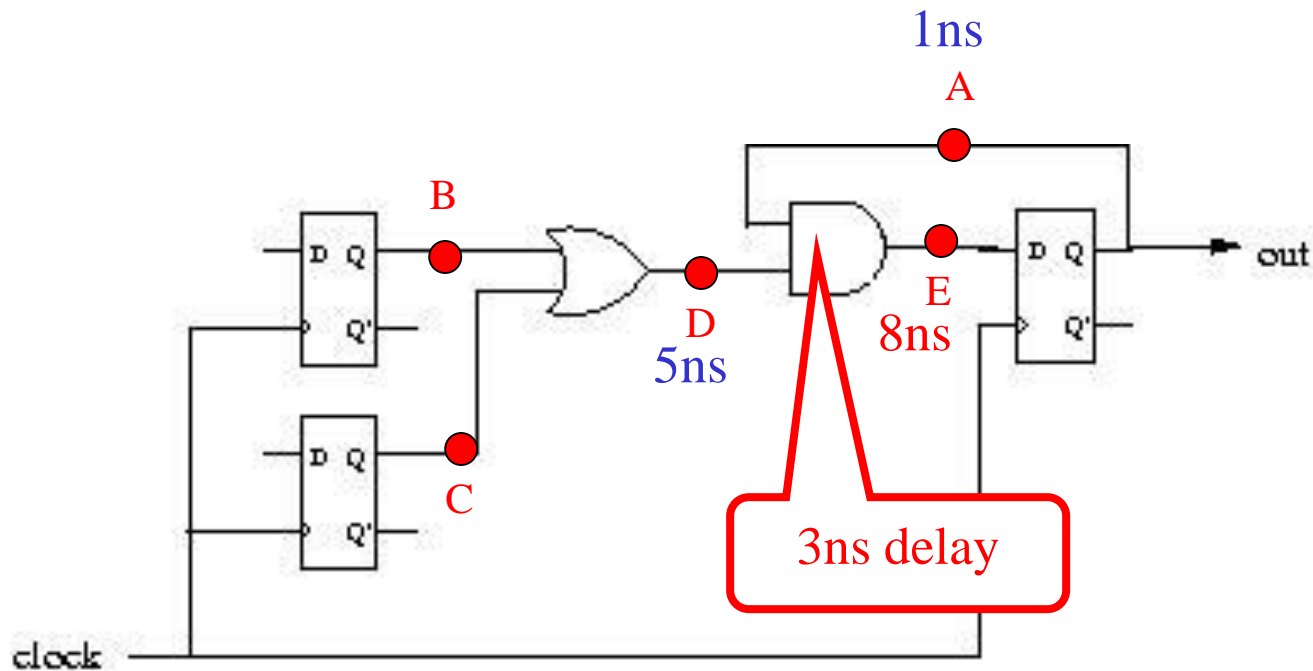- delay of AND-gate: 3 ns
- delay of OR-gate: 4 ns
- setup time of D-FF: 2 ns
- clock-to-output time of D-FF: 1 ns




Timing analysis

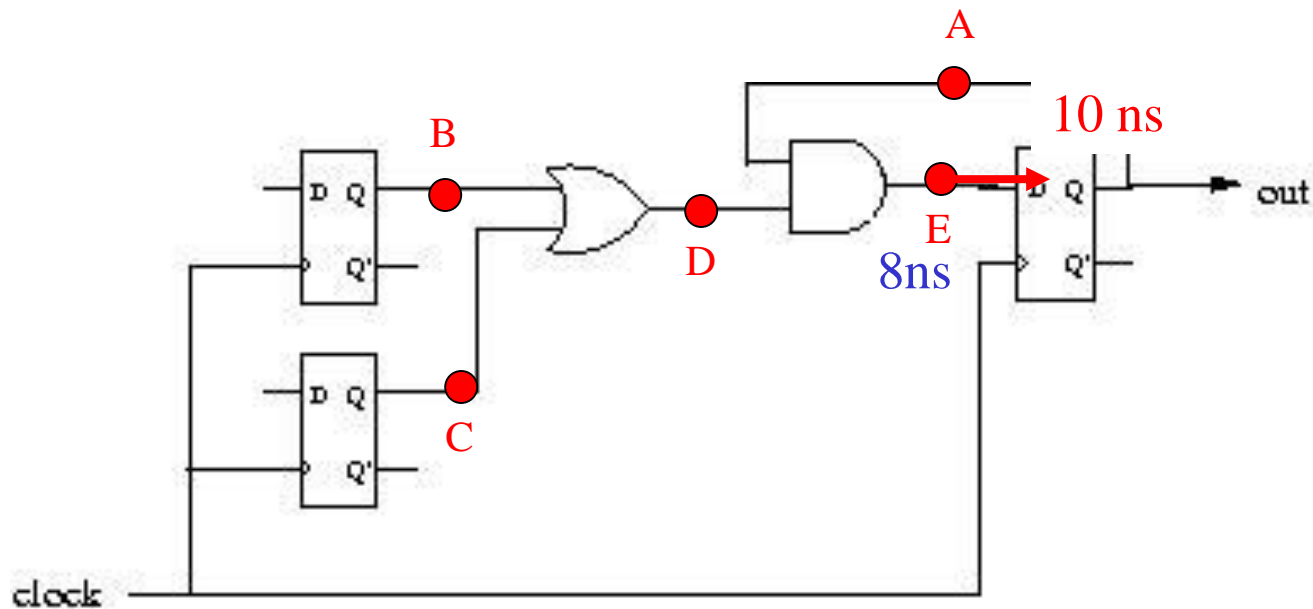
- delay of AND-gate: 3 ns
- delay of OR-gate: 4 ns
- setup time of D-FF: 2 ns
- clock-to-output time of D-FF: 1 ns



Clock period time and frequency

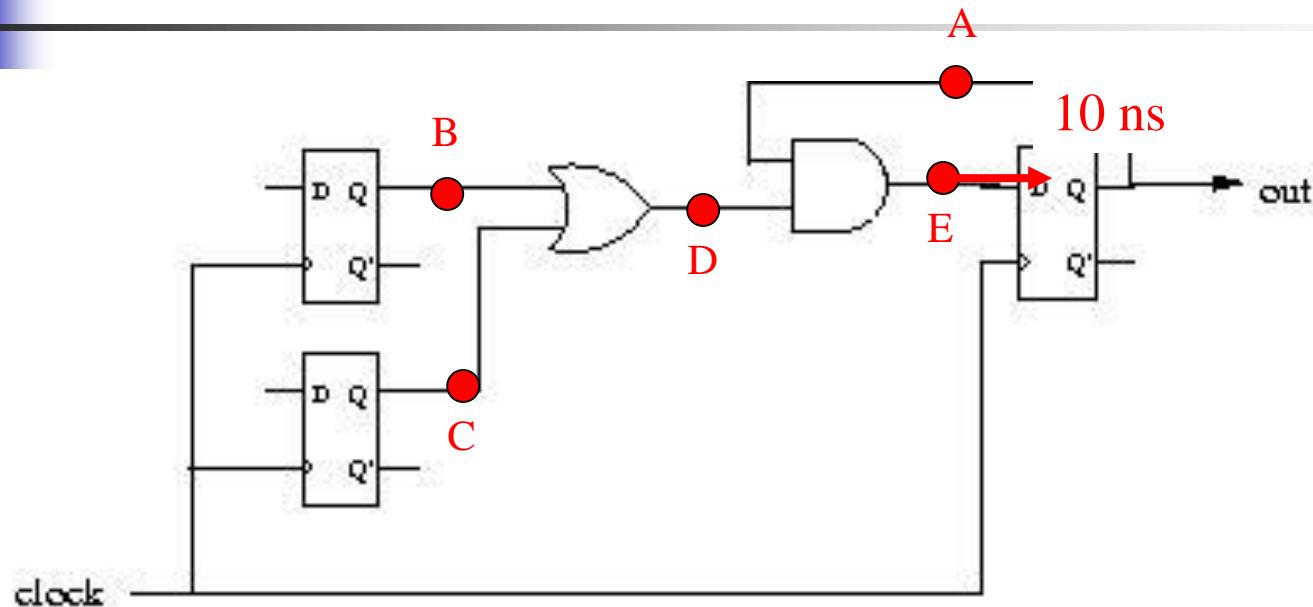
 
$$frequency \leq \frac{1}{10ns} = 100MHz$$







The next lecture

Next Lecture

  - circuit design to realize a state-diagram
 - Section 5-5





Your work before the next meeting

- Preview the textbook: **Section 5-5**
- Review “**digital circuit**”: combinational circuit design from the truth table
 - Chap. 2: Boolean algebra
 - Chap. 3: K-map simplification
- Review “**discrete mathematics**”: finite automata
 - also named finite-state machine